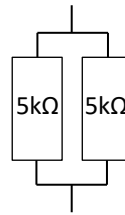


Circuit Problems


Combining Resistors

1. What is the total resistance of these two resistors?




..... $\text{k}\Omega$

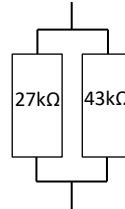2. What is the total resistance of these two resistors?




..... $\text{k}\Omega$

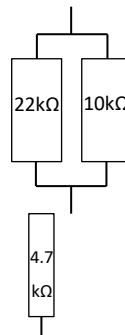3. What is the total resistance of these three resistors?




..... $\text{k}\Omega$

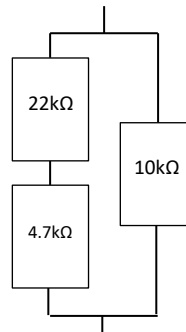4. What is the total resistance of these three resistors?




..... $\text{k}\Omega$

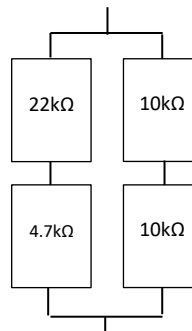5. What is the total resistance of these four resistors?




..... $\text{k}\Omega$

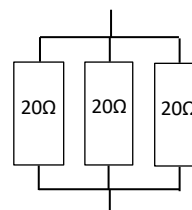6. What is the total resistance of these three resistors?




..... Ω

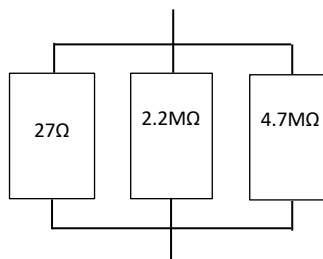7. What is the total resistance of these three resistors?




..... Ω

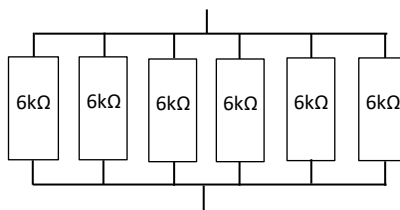8. What is the total resistance of these six resistors?




..... $k\Omega$

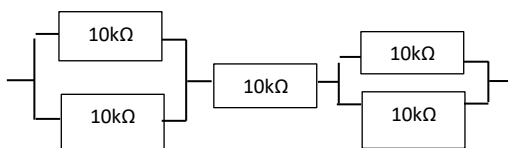9. What is the total resistance of these five resistors?




..... $k\Omega$

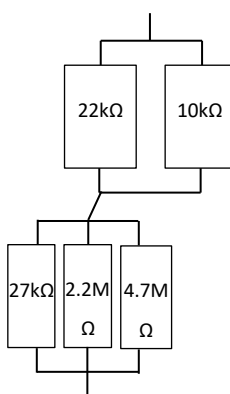10. What is the total resistance of these five resistors?



..... $k\Omega$

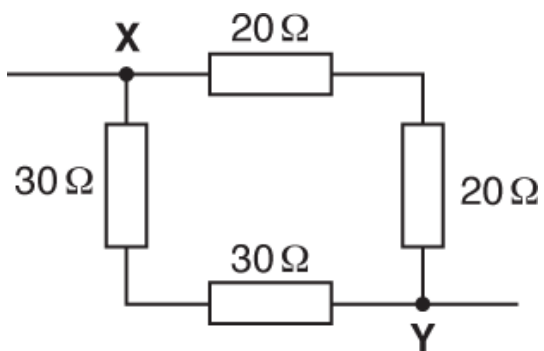11. The diagram below shows a circuit connected by a student.




What is the total resistance of the circuit between points X and Y?

- A $24\ \Omega$
- B $29\ \Omega$
- C $38\ \Omega$
- D $100\ \Omega$


Calculate the missing currents, voltages and resistances.

1.

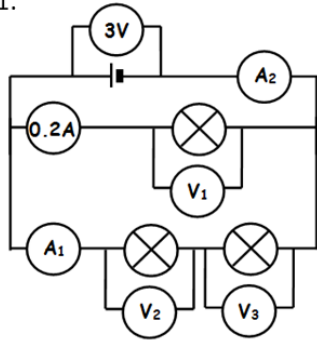


A1 = _____
A2 = _____
V1 = _____
V2 = _____
V3 = _____

2.

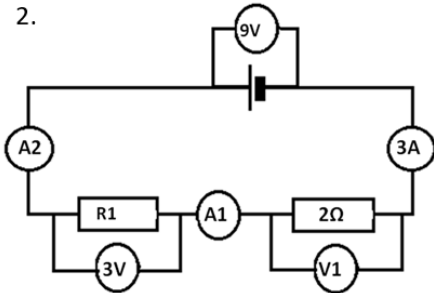


A1 = _____
A2 = _____
V1 = _____
R1 = _____

3.

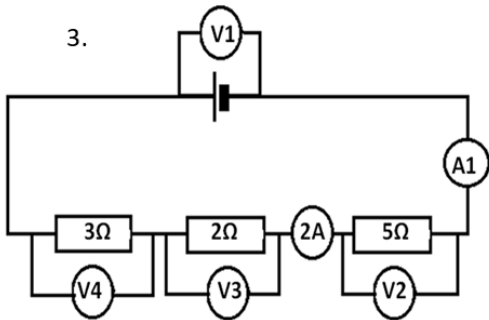


A1 = _____
V1 = _____
V2 = _____
V3 = _____
V4 = _____

4.

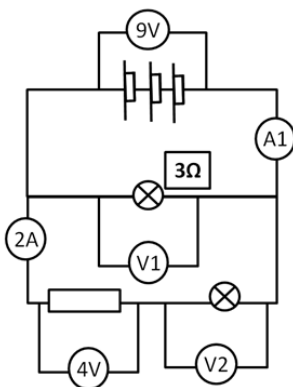


A1 = _____
V1 = _____
V2 = _____
Calculate the resistance of:
The bulb = _____
The resistor = _____

5.

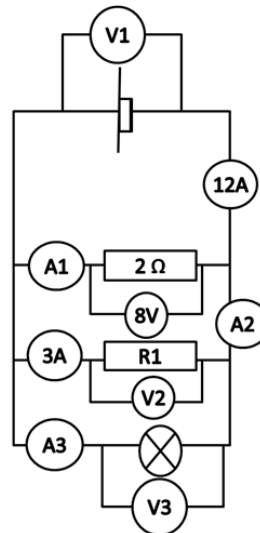


A1 = _____
A2 = _____
A3 = _____
V1 = _____
V2 = _____
V3 = _____
R1 = _____

6.

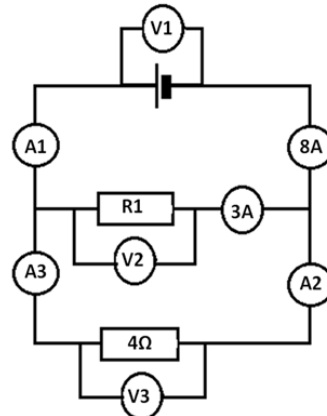

A1 = _____
A2 = _____
A3 = _____
V1 = _____
V2 = _____
R1 = _____
R2 = _____

7.

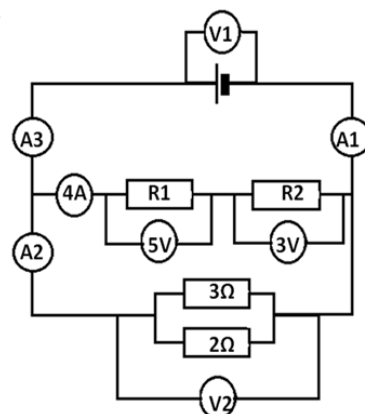

A1 = _____
A2 = _____
A3 = _____
V1 = _____
V2 = _____
V3 = _____
R1 = _____